

REPORT ON ALARM CLOCK

NAME: RITHISH KUMAR R S

REG NO: 21BEC2521

DATE OF SUBMISSION: 05-10-2023

COURSE NAME: RISCv(DM+DI)

RTL CODE:

COUNTER:

```
module counter (clk,
                reset,
                one_minute,
                load_new_c,
                new_current_time_ms_hr,
                new_current_time_ms_min,
                new_current_time_ls_hr,
                new_current_time_ls_min,
                current_time_ms_hr,
                current_time_ms_min,
                current_time_ls_hr,
                current_time_ls_min);
// Define input and output port directions
input clk,
    reset,
    one_minute,
    load_new_c;

input[3:0] new_current_time_ms_hr,
    new_current_time_ms_min,
    new_current_time_ls_hr,
    new_current_time_ls_min;

output [3:0] current_time_ms_hr,
    current_time_ms_min,
    current_time_ls_hr,
```

```

        current_time_ls_min;

// Define register to store current time
reg [3:0] current_time_ms_hr,
        current_time_ms_min,
        current_time_ls_hr,
        current_time_ls_min;

// Lodable Binary up synchronous Counter logic
/*****

// Write an always block with asynchronous reset
always@( posedge clk or posedge reset)

begin
    // Check for reset signal and upon reset load the current_time register with default value (1'b0)
    if(reset)
        begin
            current_time_ms_hr <= 4'd0;
            current_time_ms_min <= 4'd0;
            current_time_ls_hr <= 4'd0;
            current_time_ls_min <= 4'd0;
        end

    // Else if there is no reset, then check for load_new_c signal and load new_current_time to
    current_time register
    else if(load_new_c)
        begin
            current_time_ms_hr <= new_current_time_ms_hr;           // Corner cases: ms_hr
ls_hr :ms_min ls_min
            current_time_ms_min <= new_current_time_ms_min;         //      2   3   5   9
-> 00:00
            current_time_ls_hr <= new_current_time_ls_hr;           //      0   9   5   9 ->
10:00
            current_time_ls_min <= new_current_time_ls_min;         //      0   0   5   9 ->
01:00

```

```

end                                //      0   0   0   9 -> 00:10

// Else if there is no load_new_c signal, then check for one_minute signal and implement the
counting algorithm

else if (one_minute == 1)
begin
// Check for the corner case
// If the current_time is 23:59, then the next current_time will be 00:00
if(current_time_ms_hr == 4'd2 && current_time_ms_min == 4'd5 &&
current_time_ls_hr == 4'd3 && current_time_ls_min == 4'd9)
begin
current_time_ms_hr <= 4'd0;
current_time_ms_min <= 4'd0;
current_time_ls_hr <= 4'd0;
current_time_ls_min <= 4'd0;
end
// Else check if the current_time is 09:59, then the next current_time will be 10:00
else if(current_time_ls_hr == 4'd9 && current_time_ms_min == 4'd5
&& current_time_ls_min == 4'd9)
begin
current_time_ms_hr <= current_time_ms_hr + 1'd1;
current_time_ls_hr <= 4'd0;
current_time_ms_min <= 4'd0;
current_time_ls_min <= 4'd0;
end
// Else check if the time represented by minutes is 59, Increment the LS_HR by 1 and set MS_MIN
and LS_MIN to 1'b0
else if (current_time_ms_min == 4'd5 && current_time_ls_min == 4'd9)
begin
current_time_ls_hr <= current_time_ls_hr + 1'd1;
current_time_ms_min <= 4'd0;
current_time_ls_min <= 4'd0;
end
end

```

```

// Else check if the LS_MIN is equal to 9, Increment the MS_MIN by 1 and set MS_MIN to 1'b0
    else if(current_time_ls_min == 4'd9)
        begin
            current_time_ms_min <= current_time_ms_min + 1'd1;
            current_time_ls_min <= 4'd0;
        end
// Else just increment the LS_MIN by 1
    else
        begin
            current_time_ls_min <= current_time_ls_min + 1'b1;
        end
    end
end
end

endmodule

```

FSM:

```

module fsm (clock,
    reset,
    one_second,
    time_button,
    alarm_button,
    key,
    reset_count,
    load_new_a,
    show_a,
    show_new_time,
    load_new_c,
    shift);

```

```

// Define the input and output port direction
input clock,

    reset,

    one_second,

    time_button,

    alarm_button;

input [3:0] key;

output load_new_a,

    show_a,

    show_new_time,

    load_new_c,

    shift,

    reset_count;

// Define internal register for present state and next state
reg [2:0] pre_state,next_state;

// Define internal signal for timeout logic
wire time_out;

// Define registers for counting 10 secs in KEY_ENTRY and KEY_WAITED state
reg [3:0] count1,count2;

//states definition
parameter SHOW_TIME      = 3'b000;
parameter KEY_ENTRY      = 3'b001;
parameter KEY_STORED     = 3'b010;
parameter SHOW_ALARM     = 3'b011;
parameter SET_ALARM_TIME = 3'b100;
parameter SET_CURRENT_TIME = 3'b101;
parameter KEY_WAITED     = 3'b110;

```

```
parameter NOKEY      = 10;
```

```
//Counts 10 seconds pulses for KEY_ENTRY state
```

```
always @ (posedge clock or posedge reset)
```

```
begin
```

```
    // Upon reset, set the count1 value to 1'b0
```

```
    if(reset)
```

```
        count1 <= 4'd0;
```

```
    // Else check if present state is a state other than KEY_ENTRY, then set the count1 value to 1'b0
```

```
    else if(!(pre_state == KEY_ENTRY))
```

```
        count1 <= 4'd0;
```

```
    // Else check if the count1 value reaches 'd9, then set the count1 to 1'b0
```

```
    else if (count1==9)
```

```
        count1 <= 4'd0;
```

```
    // Else increment the count for every one_second pulse
```

```
    else if(one_second)
```

```
        count1 <= count1 + 1'b1;
```

```
end
```

```
//Counts 10 seconds pulses for KEY_WAITED state
```

```
always @ (posedge clock or posedge reset)
```

```
begin
```

```
    // Upon reset, set the count2 value to 1'b0
```

```
    if(reset)
```

```
        count2 <= 4'd0;
```

```
    // Else check if present state is a state other than KEY_WAITED, then set the count2 value to 1'b0
```

```
    else if(!(pre_state == KEY_WAITED))
```

```
        count2 <= 4'd0;
```

```
    // Else check if the count2 value reaches 'd9, then set the count2 to 1'b0
```

```
    else if (count2==9)
```

```
        count2 <= 4'd0;
```

```

// Else increment the count for every one_second pulse
else if(one_second)
    count2 <= count2 + 1'b1;
end

//Time out logic // Assert time_out signal whenever the count1 or count2 reaches 'd9
assign time_out=((count1==9) || (count2==9)) ? 0 : 1;

//Present state logic
always @ (posedge clock or posedge reset)
begin
    // Upon reset, assign the present_state as "SHOW_TIME"
    if(reset)
        pre_state <= SHOW_TIME;
    // Else if there is no reset then assign the present_state as next_state
    else
        pre_state <= next_state;
end

//Next state logic
// Whenever there is a change in input, check for present_state and assign next_state with
appropriate state
always @ (pre_state or key or alarm_button or time_button or time_out)
begin
    case(pre_state)
        // State transition from SHOW_TIME to other state
        SHOW_TIME : begin
            // Check if alarm_button is pressed, then the next state is SHOW_ALARM
            if (alarm_button)
                next_state = SHOW_ALARM;
            // Else check if the key is pressed or not, If key pressed, then next_state is KEY_STORED

```

```

        else if (key != NOKEY)
            next_state = KEY_STORED;
        // Else if the key is not pressed, then next_state is SHOW_TIME state
        else
            next_state = SHOW_TIME;
        end

// In KEY_STORED state assign next_state as KEY_WAITED
KEY_STORED : next_state = KEY_WAITED;
// State transition from KEY_WAITED state
KEY_WAITED : begin
    // Check if the pressed key is released, If the key is released then next_state is
KEY_ENTRY state
    if (key == NOKEY)
        next_state = KEY_ENTRY;
    // Else check if active low time_out signal is asserted, If asserted, then next_state is
SHOW_TIME state
    else if(time_out == 0)
        next_state = SHOW_TIME;
    // Else the next_state is KEY_WAITED state
    else
        next_state = KEY_WAITED;
    end

// State transition from KEY_ENTRY state
KEY_ENTRY : begin
    // Check if the alarm_button is pressed, if pressed then set the next_state as
SET_ALARM_TIME state
    if (alarm_button)
        next_state = SET_ALARM_TIME;
    // Else if the time_button is pressed, then set the next_state as SET_CURRENT_TIME state
    else if (time_button)
        next_state = SET_CURRENT_TIME;
    // Else if 10sec timeout is asserted, then set the next_state as SHOW_TIME state

```



```

        else if (time_out == 0)
            next_state = SHOW_TIME;
        // Else if the key is pressed, then set the next_state as KEY_STORED state
        else if (key != NOKEY)
            next_state = KEY_STORED;
        // Else the next_state is KEY_ENTRY state
        else
            next_state = KEY_ENTRY;
        end

    // State transition from SHOW_ALARM state
    SHOW_ALARM : begin
        // If alarm_button is pressed, then set next_state as SHOW_ALARM state else next_state
is SHOW_TIME state
        if (!alarm_button)
            next_state = SHOW_TIME;
        else
            next_state = SHOW_ALARM;
        end

    // In SET_ALARM_TIME state assign next_state as SHOW_TIME
    SET_ALARM_TIME : next_state = SHOW_TIME;

    // In SET_ALARM_TIME state assign next_state as SHOW_TIME
    SET_CURRENT_TIME : next_state = SHOW_TIME;

    // Set default state as SHOW_TIME state
    default : next_state = SHOW_TIME;

endcase
end

//Moore FSM outputs

// Assert show_new_time signal, when present state is either KEY_ENTRY or KEY_STORED or
KEY_WAITED state

```

```

assign show_new_time = (pre_state == KEY_ENTRY ||
                        pre_state == KEY_STORED ||
                        pre_state == KEY_WAITED) ? 1 : 0;

// Assert show_a signal when present state is SHOW_ALARM
assign show_a      = (pre_state == SHOW_ALARM) ? 1 : 0;

// Assert load_new_a signal when present state is SET_ALARM_TIME state
assign load_new_a  = (pre_state == SET_ALARM_TIME) ? 1 : 0;

// Assert load_new_c signal when present state is SET_CURRENT_TIME state
assign load_new_c  = (pre_state == SET_CURRENT_TIME) ? 1 : 0;

// Assert reset_count signal when present state is SET_CURRENT_TIME state
assign reset_count = (pre_state == SET_CURRENT_TIME) ? 1 : 0;

// Assert shift signal when present state is KEY_STORED state
assign shift      = (pre_state == KEY_STORED) ? 1 : 0;

endmodule

```

KEYREG:

```

module keyreg(reset,
              clock,
              shift,
              key,
              key_buffer_ls_min,
              key_buffer_ms_min,
              key_buffer_ls_hr,
              key_buffer_ms_hr);

// Define input and output port direction
input reset,
       clock,
       shift;

```

```
input [3:0] key;
output reg [3:0] key_buffer_ls_min,
               key_buffer_ms_min,
               key_buffer_ls_hr,
               key_buffer_ms_hr;
```

```
////////////////////////////////////////////////////////////////
```

```
// This procedure stores the last 4 keys pressed. The FSM block
// detects the new key value and triggers the shift pulse to shift
// in the new key value.
```

```
////////////////////////////////////////////////////////////////
```

```
always @(posedge clock or posedge reset)
begin
    // For asynchronous reset, reset the key_buffer output register to 1'b0
    if (reset)
    begin
        key_buffer_ls_min <= 0;
        key_buffer_ms_min <= 0;
        key_buffer_ls_hr <= 0;
        key_buffer_ms_hr <= 0;
    end
    // Else if there is a shift, perform left shift from LS_MIN to MS_HR
    else if (shift == 1)
    begin
        key_buffer_ms_hr <= key_buffer_ls_hr;
        key_buffer_ls_hr <= key_buffer_ms_min;
        key_buffer_ms_min <= key_buffer_ls_min;
        key_buffer_ls_min <= key;
    end
end
```

```
end
```

```
endmodule
```

LCDDRIVE:

```
module lcd_driver (alarm_time,
                   current_time,
                   show_alarm,
                   show_new_time,
                   key,display_time,
                   sound_alarm);

//Define input and output ports direction
input [3:0] key;
input [3:0]alarm_time;
input [3:0]current_time;
input show_alarm;
input show_new_time;


output reg [7:0]display_time;
output reg sound_alarm;


//Define the internal signals
reg [3:0]display_value ;


//Define the Parameter constants to represent LCD numbers
parameter ZERO  = 8'h30;
parameter ONE   = 8'h31;
```

```
parameter TWO   = 8'h32;
parameter THREE = 8'h33;
parameter FOUR  = 8'h34;
parameter FIVE  = 8'h35;
parameter SIX   = 8'h36;
parameter SEVEN = 8'h37;
parameter EIGHT = 8'h38;
parameter NINE  = 8'h39;
parameter ERROR = 8'h3A;
```

```
always @ (alarm_time or current_time or show_alarm or show_new_time or key)
```

```
begin
```

```
    //Displays the key_time,alarm_time or current_time as per the control signals
```

```
    if (show_new_time)
```

```
        display_value = key;
```

```
    else if (show_alarm)
```

```
        display_value = alarm_time;
```

```
    else
```

```
        display_value = current_time;
```

```
    //Generates sound_alarm logic i,e when current_time is equal to alarm_time
```

```
    if (current_time == alarm_time)
```

```
        sound_alarm = 1'b1;
```

```
    else
```

```
        sound_alarm = 1'b0;
```

```
end
```

```
//Decoder logic
```

```
always @ (display_value)
```

```
begin
  case (display_value)
    4'd0 : display_time = ZERO;
    4'd1 : display_time = ONE;
    4'd2 : display_time = TWO;
    4'd3 : display_time = THREE;
    4'd4 : display_time = FOUR;
    4'd5 : display_time = FIVE;
    4'd6 : display_time = SIX;
    4'd7 : display_time = SEVEN;
    4'd8 : display_time = EIGHT;
    4'd9 : display_time = NINE;
    default : display_time = ERROR;
  endcase
end
```

```
endmodule
```

LCDDRIVER_4:

```
module lcd_driver_4 ( alarm_time_ms_hr,
                      alarm_time_ls_hr,
                      alarm_time_ms_min,
                      alarm_time_ls_min,
                      current_time_ms_hr,
                      current_time_ls_hr,
                      current_time_ms_min,
                      current_time_ls_min,
                      key_ms_hr,
                      key_ls_hr,
                      key_ms_min,
```

```
        key_ls_min,
        show_a,
        show_current_time,
        display_ms_hr,
        display_ls_hr,
        display_ms_min,
        display_ls_min,
        sound_a);

// Define input and output port directions
input [3:0] alarm_time_ms_hr,
        alarm_time_ls_hr,
        alarm_time_ms_min,
        alarm_time_ls_min,
        current_time_ms_hr,
        current_time_ls_hr,
        current_time_ms_min,
        current_time_ls_min,
        key_ms_hr,
        key_ls_hr,
        key_ms_min,
        key_ls_min;

input show_a,
        show_current_time;

output [7:0] display_ms_hr,
           display_ls_hr,
           display_ms_min,
           display_ls_min;

output sound_a;
```

```
wire sound_alarm1,sound_alarm2,sound_alarm3,sound_alarm4;

// Assert sound_a when all 4 digits matches

assign sound_a = sound_alarm1 & sound_alarm2 & sound_alarm3 & sound_alarm4 ;


//Instantiate lcd_driver as MS_HR_display
lcd_driver MS_HR (.alarm_time(alarm_time_ms_hr),
    .current_time(current_time_ms_hr),
    .key(key_ms_hr),
    .show_alarm(show_a),
    .show_new_time(show_current_time),
    .display_time(display_ms_hr),
    .sound_alarm(sound_alarm1));

//Instantiate lcd_driver as LS_HR_display
lcd_driver LS_HR (.alarm_time(alarm_time_ls_hr),
    .current_time(current_time_ls_hr),
    .key(key_ls_hr),
    .show_alarm(show_a),
    .show_new_time(show_current_time),
    .display_time(display_ls_hr),
    .sound_alarm(sound_alarm2));


//Instantiate lcd_driver as MS_MIN_display
lcd_driver MS_MIN (.alarm_time(alarm_time_ms_min),
    .current_time(current_time_ms_min),
    .key(key_ms_min),
    .show_alarm(show_a),
    .show_new_time(show_current_time),
    .display_time(display_ms_min),
    .sound_alarm(sound_alarm3));
```



```
//Instantiate lcd_driver as LS_MIN_display
lcd_driver LS_MIN(.alarm_time(alarm_time_ls_min),
    .current_time(current_time_ls_min),
    .key(key_ls_min),
    .show_alarm(show_a),
    .show_new_time(show_current_time),
    .display_time(display_ls_min),
    .sound_alarm(sound_alarm4));

endmodule
```

TIMEGEN:

```
module timegen(clock,
    reset,
    reset_count,
    fastwatch,
    one_second,
    one_minute
);
// Define input and output port directions
input clock,
    reset,
    reset_count, //Resets the timegen whenever a new current time is set
    fastwatch;

output one_second,
    one_minute;

// Define internal registers required
reg [13:0] count;
reg one_second;
```

```
reg one_minute_reg;
```

```
reg one_minute;
```

```
//One minute pulse generation
```

```
always@(posedge clock or posedge reset)
```

```
begin
```

```
    // Upon reset, set the one_minute_reg value to zero
```

```
    if (reset)
```

```
    begin
```

```
        count<=14'b0;
```

```
        one_minute_reg<=0;
```

```
    end
```

```
    // Else check if there is a reset from alarm controller and reset the one_minute_reg and count value
```

```
    else if (reset_count)
```

```
    begin
```

```
        count<=14'b0;
```

```
        one_minute_reg<=1'b0;
```

```
    end
```

```
    // Else check if the count value reaches 'd15359 to generate 1 minute pulse
```

```
    else if (count[13:0]== 14'd15359)
```

```
    begin
```

```
        count<=14'b0;
```

```
        one_minute_reg<=1'b1;
```

```
    end
```

```
    // Else for every posedge of clock just increment the count.
```

```
    else
```

```
    begin
```

```
        count<=count+1'b1;
```

```
        one_minute_reg<=1'b0;
```

```

    end

end

//One second pulse generation
always@(posedge clock or posedge reset)
begin
    // If reset is asserted, set one_second and counter_sec value to zero
    if (reset)
    begin
        one_second<=1'b0;
    end

    // Else check if there is reset from alarm_controller, and reset the one_second and counter_sec
    value
    else if (reset_count)
    begin
        one_second<=1'b0;
    end

    // Else check if the count value reaches the 'd255 to generate and count 1 sec pulse
    else if (count[7:0]==8'd255)
    begin
        one_second<=1'b1;
    end

    // Else set the one_second and counter_sec value to zero
    else
    begin
        one_second<=1'b0;
    end
end

//Fastwatch Mode Logic that makes the counting faster

```

```

always@(*)
begin
    // If fastwatch is asserted, make one_second equivalent to one_minute
    if(fastwatch)
        one_minute =one_second;
    // Else assert one_minute signal when one_minute_reg is asserted
    else
        one_minute =one_minute_reg;
    end

endmodule

```

ALARM_REG:

```

module alarm_reg (new_alarm_ms_hr,
    new_alarm_ls_hr,
    new_alarm_ms_min,
    new_alarm_ls_min,
    load_new_alarm,
    clock,
    reset,
    alarm_time_ms_hr,
    alarm_time_ls_hr,
    alarm_time_ms_min,
    alarm_time_ls_min );

    // Define input and output port directions
    input [3:0]new_alarm_ms_hr,
        new_alarm_ls_hr,
        new_alarm_ms_min,
        new_alarm_ls_min;

```

```

input load_new_alarm;

input clock;

input reset;


output reg [3:0] alarm_time_ms_hr,
             alarm_time_ls_hr,
             alarm_time_ms_min,
             alarm_time_ls_min;


//Lodable Register which stores alarm time
always @ (posedge clock or posedge reset)
begin
    // Upon reset, store reset value(1'b0) to the alarm_time registers
    if(reset)
    begin
        alarm_time_ms_hr <= 4'b0;
        alarm_time_ls_hr <= 4'b0;
        alarm_time_ms_min <= 4'b0;
        alarm_time_ls_min <= 4'b0;
    end
    // If no reset, check for load_new_alarm signal and load new_alarm time to alarm_time registers
    else if(load_new_alarm)
    begin
        alarm_time_ms_hr <= new_alarm_ms_hr;
        alarm_time_ls_hr <= new_alarm_ls_hr;
        alarm_time_ms_min <= new_alarm_ms_min;
        alarm_time_ls_min <= new_alarm_ls_min;
    end
end

endmodule

```

ALARM_CLOCK_TOP:

```
module alarm_clock_top(clock,
    key,
    reset,
    time_button,
    alarm_button,
    fastwatch,
    ms_hour,
    ls_hour,
    ms_minute,
    ls_minute,
    alarm_sound);

// Define port directions for the signals
input clock,
    reset,
    time_button,
    alarm_button,
    fastwatch;

input [3:0] key;

output [7:0] ms_hour,
    ls_hour,
    ms_minute,
    ls_minute;

output alarm_sound;

//Define the Interconnecting internal wires
wire one_second,
    one_minute,
```

```
load_new_c,  
load_new_a,  
show_current_time,  
show_a,  
shift,  
reset_count;
```

```
wire [3:0] key_buffer_ms_hr,  
          key_buffer_ls_hr,  
          key_buffer_ms_min,  
          key_buffer_ls_min,  
          current_time_ms_hr,  
          current_time_ls_hr,  
          current_time_ms_min,  
          current_time_ls_min,  
          alarm_time_ms_hr,  
          alarm_time_ls_hr,  
          alarm_time_ms_min,  
          alarm_time_ls_min;
```

```
//Instantiate lower sub-modules. Use interconnect(Internal) signals for connecting the sub modules
```

```
// Instantiate the timing generator module
```

```
timegen tgen1 (.clock(clock),  
              .reset(reset),  
              .fastwatch(fastwatch),  
              .one_second(one_second),  
              .one_minute(one_minute),  
              .reset_count(reset_count));
```

```
// Instantiate the counter module
```

```

counter count1 (.one_minute(one_minute),
    .new_current_time_ms_min(key_buffer_ms_min),
    .new_current_time_ls_min(key_buffer_ls_min),
    .new_current_time_ms_hr(key_buffer_ms_hr),
    .new_current_time_ls_hr(key_buffer_ls_hr),
    .load_new_c(load_new_c),
    .clk(clock),
    .reset(reset),
    .current_time_ms_min(current_time_ms_min),
    .current_time_ls_min(current_time_ls_min),
    .current_time_ms_hr(current_time_ms_hr),
    .current_time_ls_hr(current_time_ls_hr)
);

```

// Instantiate the alarm register module

```

alarm_reg alreg1 (.new_alarm_ms_hr(key_buffer_ms_hr),
    .new_alarm_ls_hr(key_buffer_ls_hr),
    .new_alarm_ms_min(key_buffer_ms_min),
    .new_alarm_ls_min(key_buffer_ls_min),
    .load_new_alarm(load_new_a),
    .clock(clock),
    .reset(reset),
    .alarm_time_ms_hr(alarm_time_ms_hr),
    .alarm_time_ls_hr(alarm_time_ls_hr),
    .alarm_time_ms_min(alarm_time_ms_min),
    .alarm_time_ls_min(alarm_time_ls_min));

```

// Instantiate the key register module

```

keyreg keyreg1(.reset(reset),
    .clock(clock),
    .shift(shift),

```



```
.key(key),  
.key_buffer_ls_min(key_buffer_ls_min),  
.key_buffer_ms_min(key_buffer_ms_min),  
.key_buffer_ls_hr(key_buffer_ls_hr),  
.key_buffer_ms_hr(key_buffer_ms_hr)  
);
```

// Instantiate the FSM controller

```
fsm fsm1 (.clock(clock),  
.reset(reset),  
.one_second(one_second),  
.time_button(time_button),  
.alarm_button(alarm_button),  
.key(key),  
.load_new_a(load_new_a),  
.show_a(show_a),  
.reset_count(reset_count),  
.show_new_time(show_current_time),  
.load_new_c(load_new_c),  
.shift(shift)  
);
```

// Instantiate the lcd_driver_4 module

```
lcd_driver_4 lcd_disp (.alarm_time_ms_hr(alarm_time_ms_hr),  
.alarm_time_ls_hr(alarm_time_ls_hr),  
.alarm_time_ms_min(alarm_time_ms_min),  
.alarm_time_ls_min(alarm_time_ls_min),  
.current_time_ms_hr(current_time_ms_hr),  
.current_time_ls_hr(current_time_ls_hr),  
.current_time_ms_min(current_time_ms_min),  
.current_time_ls_min(current_time_ls_min),  
.key_ms_hr(key_buffer_ms_hr),
```

```
.key_ls_hr(key_buffer_ls_hr),  
.key_ms_min(key_buffer_ms_min),  
.key_ls_min(key_buffer_ls_min),  
.show_a(show_a),  
.show_current_time(show_current_time),  
.display_ms_hr(ms_hour),  
.display_ls_hr(ls_hour),  
.display_ms_min(ms_minute),  
.display_ls_min(ls_minute),  
.sound_a(alarm_sound));
```

```
endmodule
```

ALARM_CLOCK_TB:

```
module tb_alarm_clock();
```

```
    reg clk,  
        reset,  
        fast_watch,  
        alarm_button,  
        time_button;
```

```
    reg [3:0] key;
```

```
    wire [7:0] display_ms_hr,  
        display_ms_min,  
        display_ls_hr,  
        display_ls_min;
```

```
wire sound_alarm;
```

```
parameter cycle = 2;
```

```
alarm_clock_top DUV(.clock(clk),  
    .reset(reset),  
    .fastwatch(fast_watch),  
    .alarm_button(alarm_button),  
    .time_button(time_button),  
    .key(key),  
    .alarm_sound(sound_alarm),  
    .ms_hour(display_ms_hr),  
    .ls_hour(display_ls_hr),  
    .ms_minute(display_ms_min),  
    .ls_minute(display_ls_min));
```

```
//Clock generation logic
```

```
initial
```

```
begin
```

```
    clk = 1'b0;
```

```
    forever
```

```
        #(cycle/2) clk = ~clk;
```

```
end
```

```
//
```

```
//Stimulus logic
```

```
initial
```

```
begin
```

```
    //Hard reset the design
```

```
reset = 1;

#10;

reset = 0;

//Set fastwatch to 1 to make counting faster
fast_watch = 1;

//Set key time to current time :11:23
key = 1;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
key = 1;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
key = 2;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
key = 3;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
time_button = 1;
@(negedge clk);
time_button = 0;

//Set key time to alarm time :11:30
```

```

key = 1;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
key = 1;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
key = 3;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
key = 0;
repeat(3)
@(negedge clk);
key = 10;
@(negedge clk);
alarm_button = 1;
@(negedge clk);
alarm_button = 0;
#(7*256*2); // 7 -> 7minutes -> 7seconds -> 7 * 256 clock cycles -> 7*256*2 (Time period of clock)
// Time out for Alarm clock
// key = 7;
repeat(4*2564) // Wait for minimum 10second pulses i.e (10*256) clock cycles
@(negedge clk);
$finish;
end


```

initial

```
$monitor($time,"\\-ns\\t MAVEN SILICON : \\tDISPLAY_MS_HR =%H >>> DISPLAY_LS_HR =%H>>>  
DISPLAY_MS_MIN =%H>>>  
DISPLAY_LS_MIN=%H",display_ms_hr[3:0],display_ls_hr[3:0],display_ms_min[3:0],display_ls_min[3:  
0]);
```

endmodule

WAVE FORM:

 

SYNTHESIS:

